

2021 DCS 期末考

第一題：

Note. In the following, you don't need to write a full Verilog/SystemVerilog code module to illustrate your answers. Just a piece of code is enough.

- a (2%)What is the difference between == and ===? Use a short example to show your answers.
- b. (2%)What is the difference between = assignment and <= assignment? Use a short example to show your answers.
- c. (4%)Write two coding style examples for combinational circuit.
- d. (2%)What do the terms “wire”, “reg” and “logic” in Verilog refer to?

第二題：

(10%) For the following timing report, please draw its register-to-register timing path labeled by a to f in the figure. (Note. You can combine all combinational logic delay into one delay.)


a. answer for path a

Startpoint: modem/qr_tmp (rising edge-triggered flip-flop clocked by Sysclk altpll clk[2])		
Endpoint: modem/qr (rising edge-triggered flip-flop clocked by Sysclk altpll clk[2])		
Path Group: Sysclk altpll clk[2]		
Path Type: max		
Point	Incr	Path

clock Sysclk altpll clk[2] (rise edge)	0.000	0.000
clock network delay (propagated)	0.204	0.204
modem/qr_tmp/CLK (DFF_D1_CLK1_NCLR1_CKEN1_RSCN1_SCIN1)	0.000	0.204 r
modem/qr_tmp/Q (DFF_D1_CLK1_NCLR1_CKEN1_RSCN1_SCIN1)	0.146 &	0.350 f
modem/qr_tmp_ASTfhInst7779/OUT (BUF_D3)	0.073 &	0.423 f
lcell_comb6052/OUT (BUF_D6)	0.166 &	0.589 f
modem/qr/D (DFF_D1_CLK1_NCLR1_RSCN1_SCIN1)	0.026 &	0.614 f
data arrival time		0.614
clock Sysclk altpll clk[2] (rise edge)	6.510	6.510
clock network delay (propagated)	0.321	6.831
clock reconvergence pessimism	0.003	6.835
inter-clock uncertainty	-0.160	6.675
modem/qr/CLK (DFF_D1_CLK1_NCLR1_RSCN1_SCIN1)		6.675 r
library setup time	-0.340	6.334
data required time		6.334

data required time		6.334
data arrival time		-0.614

slack (MET)		5.720

 

第三題:

follow question 2

answer for path b

第四題:

follow question 2

answer for path c

第五題:

follow question 2

answer for path d

第六題:

follow question 2

answer for path e

第七題:

follow question 2

answer for path f

第八題:

Note. In the following, you don't need to write a full Verilog/SystemVerilog code module to illustrate your answers. Just a piece of code is enough.

Re-write the module in behavioral form. The delays can be assumed to be gate delays

```
module expl_str(x,y,a,b,c);
    input a, b, c;
    output x, y;
    wire    a, b, c, x, y;
    wire    na, nb, nc, t3, t5, t6;

    not n1(na,a);
    not n2(nb,b);
    not n3(nc,c);
    and #1 a1(t3,na,b,c);
    and a2(t5,a,nb,c);
    and a3(t6,a,b,nc);
    or o1(x,t3,t6);
    or #3 o2(y,a,t5);

endmodule
```

第九題:

Draw a schematic showing the approximate RTL-level description generated by a synthesis program
you can draw it on a paper, take a photo, and upload

```
module whatsyn2(output [6:0] sum, input [15:0] nibbles, a, b, c);
    logic [15:0] n2;
    logic        last_c;

    always @( posedge a )
        if ( !b ) begin
            sum = 0;
        end else begin

            if ( c != last_c ) begin
                n2 = nibbles;
                for ( int i=0; i < 4; i++ ) begin
                    sum = sum + n2[3:0];
                    n2 = n2 >> 4;
                end
            end
            last_c = c;
        end

endmodule
```

第十題:

For the following code,

- (a) (2%) what is the intended function of the code
- (b) (2%) correct any bad things in the above code
- (c) (3%) Sketch a possible synthesized circuit for the code
- (d) (3%) rewrite this with assign statement

```
module block (q, I, s)
```

```
input [3:0] I;
```

```
input [1:0] s;
```

```
output q;
```

```
always @(s)
```

```
    case(s)
```

```
        00: q = i[0];
```

```
        01: q = i[1];
```

```
        10: q = i[2];
```

```
        11: q= i[3];
```

```
    endcase
```

```
endmodule
```

第十一題:

Correct any bad coding in the followings

```
module signed_adder_with_carry_in
(input  logic signed [3:0] a, b,
input  logic                ci,
output logic signed [3:0] sum,
output logic                co);

    assign {co,sum} = a + b + ci;
endmodule
```

第十二題:

show the true or false result of each if condition

```
logic a;                // 1-bit 4-state variable
logic [1:0] b;          // 2-bit 4-state variable

initial begin
    a = 1;
    b = 1;

    if (!a) ... // evaluates as
    if (~a) ... // evaluates as

    if (!b) ... // evaluates as
    if (~b) ... // evaluates as
end
```

第十三題:

Correct the following code if you intend to show "a" is true if (a==1)

```
module bar;
  reg a;
  initial begin
    a = 1;
    if (a);
      $display("'a' is true");
    else

      $display("'a' is false");
  end
endmodule
```

第十四題:

Correct the following code if you intend to connect two 1-bit adder together.

```
module adder (input  logic a, b, ci,
               output logic sum, co);

  ...
endmodule

module top;
  wire a, b, ci, s1, s2, c1;

  adder i1 (.a(a), .b(b), .ci(c1), .sum(s1), .co(c1) );
  adder i2 (.a(a), .b(b), .ci(c), .sum(s2), .co(co) );
endmodule
```

第十五題：

(10%) suppose you have a system where every problem must pass through four pipeline stages with delays of 30ns, 60ns, 15ns, 20ns.

- (a) (2%) Which stage is the bottleneck
- (b) (2%) What is the utilization rate (time spend doing useful work divided by total time) of each stage?
- (c) (3%) If each stage cannot be further pipelined, but can be replicated. How many of each module do you need to have full utilization of your system? (that is, no module should be idle after a warm up period) Draw a diagram to show your answer
- (d) (3%) If each stage cannot be replicated, but can be pipelined. What is the minimum number of stages from beginning to end in a pipeline that has no load imbalance? Draw a diagram to show your answer.


第十六題：

(setup time and hold time violation check)

you can write answer on the e3 text frame or upload your photo


For Flip-Flop A in Table 1 (used for DFF X, Y, Z) , and a 2GHz clock, check the following figure for timing violations. If there is a hold time violation, indicate

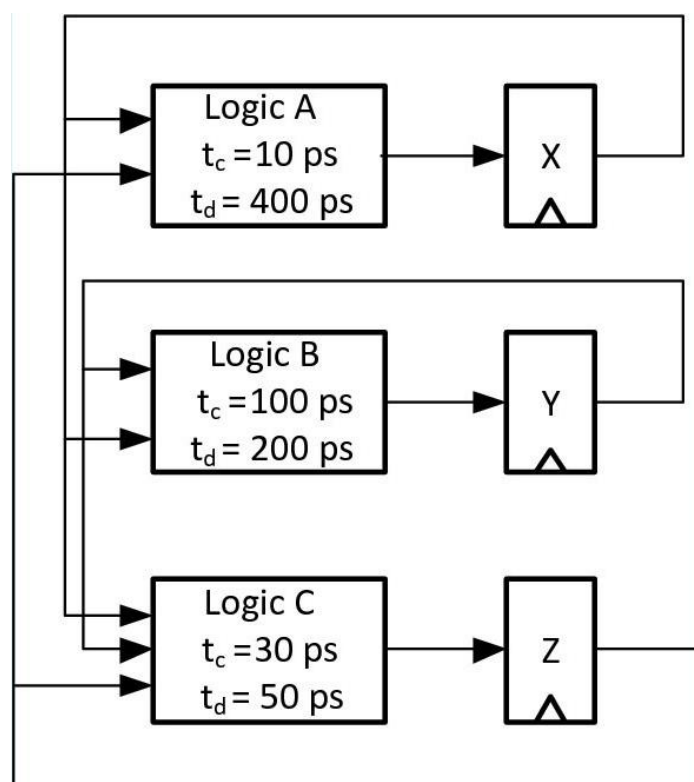- (a) (5%) where delay must be added, and the necessary delay value




Parameter (ps)	DFF A	DFF B
Setup time: t_s	20	100
Hold time: t_h	10	-20
Contamination delay, clock to q, T_{ccq}	10	2
Propagation delay, clock to q, t_{dcq}	20	30

hold time check

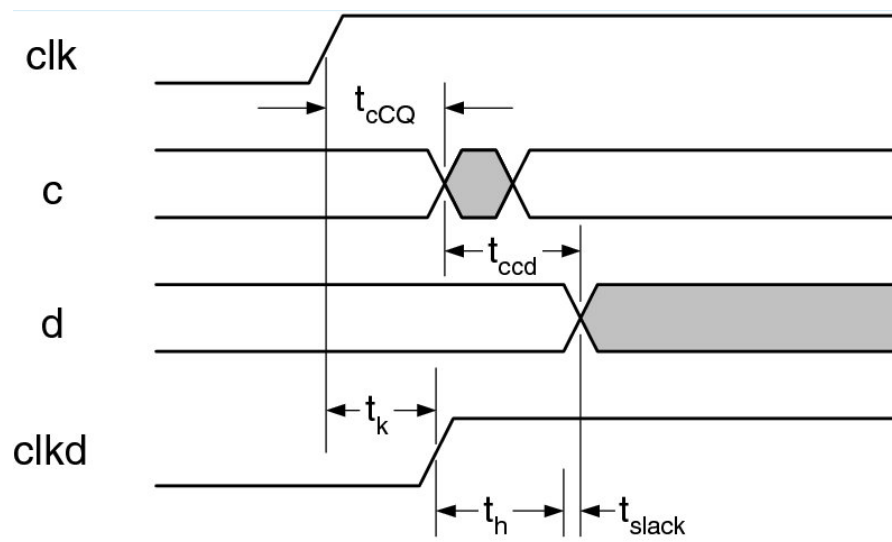

setup time check

 

第十七題:

follow question 16

(10%) recheck for setup time violation. Is it possible to run faster than 2GHz clock? Derive the cycle time for this maximum clock frequency?

第十八題 :

follow question 16

(15%) For DFF B in above Table (used for DFF X, Y, Z) and a 2GHz clock, check the figure again to see if there a setup time or hold time violation, and derive the minimum cycle time for this design.